

Basic cutset  $A(1,6)$ ,  $B(2,6)$ ,  $C(3,5)$  &  $D(4,5)$

Basic cutset element	A	B	C	D
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	1	-1
6	1	1	1	0

$B =$

$B_b = U_b$

$B_d$

$$B_{ij} = 1$$

If  $i$ th element is a part of  $j$ th cutset & direction of there is same

$$B_{ij} = -1$$

If  $i$ th element is a part of  $j$ th cutset & their directions are opposite

$$B_{ij} = 0$$


If  $i$ th element is not a part of  $j$ th cutset

The total power in primitive network is given by  
 $(j^*)^T \cdot e$

Diagonal entries of  $Z$  represents self impedance of elements & off diagonal entry of  $Z$  represents mutual impedances between the elements

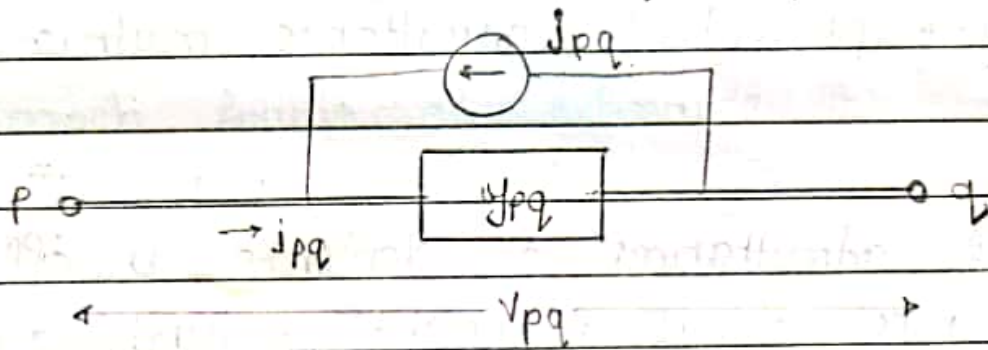2) Admittance form of representing an element

In admittance form element connected between  $P$  &  $q$  represented as,



$Y_{pq} \rightarrow$  Admittance of the element

$j_{pq} \rightarrow$  Impressed current (Source) current across the element  $p$  &  $q$

$V_{pq}$  &  $i_{pq} \rightarrow$  Voltage & current through element.

Performance eq<sup>n</sup>

$$i_{pq} + j_{pq} = Y_{pq} \cdot V_{pq}$$

Hence the performance equation in primitive

## \* Incidence Matrices

1) Element node incidence matrix  $[A]$

An element is said to be an incident on a node if the node is one terminal of the element. Thus each element is incident on two nodes



property : Addition of Any Row is zero

$$A_{ij} = 1$$

If  $j$ th element is incident on  $j$ th node & is directed away from the node

$$A_{ij} = -1$$

If  $j$ th element is incident on  $j$ th node & is directed towards the node

$$A_{ij} = 0$$

If  $j$ th element is not incident on  $j$ th node



nodes elem- ents	①	②	③	④	
1	-1	0	0	0	} $A_b$
2	1	-1	0	0	
3	0	1	0	-1	
4	0	1	-1	0	
5	0	0	1	-1	} $A_d$
6	0	0	0	-1	

from Bus incidence matrix make graph of original power system :

nodes elem- ents	①	②	③	④	⑤
1	-1	0	0	0	1
2	1	-1	0	0	0
3	0	1	0	-1	0
4	0	1	-1	0	0
5	0	0	1	-1	0
6	0	0	0	-1	1

Proof:-

i)  $A_b \cdot K^t = U$

$$K = \begin{bmatrix} -1 & -1 & -1 \\ 0 & -1 & -1 \\ 0 & 0 & -1 \end{bmatrix} \quad K^t = \begin{bmatrix} -1 & 0 & 0 \\ -1 & -1 & 0 \\ -1 & -1 & -1 \end{bmatrix}$$

$$A_b \cdot K^t = \begin{bmatrix} -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \quad \begin{bmatrix} -1 & 0 & 0 \\ -1 & -1 & 0 \\ -1 & -1 & -1 \end{bmatrix}$$

$$A_b \cdot K^t = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = U \quad \text{Hence proved}$$

ii)  $B_d \cdot A_b = A_d$

$$B_d \cdot A_b = \begin{bmatrix} 1 & 1 & 0 \\ 1 & 1 & 1 \end{bmatrix}_{2 \times 3} \quad \begin{bmatrix} -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}_{3 \times 3}$$

$$B_d \cdot A_b = \begin{bmatrix} 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} = -A_d$$

Henced proved

property  $B_b [U_b] \rightarrow$  It is a square & identity matrix

$$B_1 \cdot A_b = \begin{bmatrix} 0 & 0 & 1 & -1 \\ 1 & 1 & 1 & 0 \end{bmatrix}_{2 \times 4} \begin{bmatrix} -1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 1 & -1 & 0 \end{bmatrix}_{4 \times 4}$$

$$= \begin{bmatrix} 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & -1 \end{bmatrix} = A_1$$

Dimension of B - matrix  $e \times (n-1)$

5) Augmented cutset incidence matrix ( $B^1$ )  
dimension ( $e \times e$ )

To form this matrix fictitious (dummy) cutsets are taken on fictitious cutset involves only one link & no any branch. The columns corresponding to fictitious cutset are introduced after the basic cutset columns.

no. of fictitious cutset - no. of link



$$k_{ij} = 1$$

If  $i$ th branch is a part of  $j$ th path & its direction is same as that of path

$$k_{ij} = -1$$

If  $i$ th branch is part of  $j$ th path & its direction is opposite to path

$$k_{ij} = 0$$

If  $i$ th branch is not part of  $j$ th path

$A_b$  - Part of incidence matrix include Branch

$A_l$  - part of incidence matrix - include links

property of  $A_b$  - It is always square matrix

Relation :

$$A_b \cdot K^t = U$$

	Basic element loop +		
		D	E
$C =$	1	-1	-1
	2	-1	-1
	3	0	-1
	4	1	0
	5	0	1

$\left. \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} \right\} C_b$   
 $\left. \begin{matrix} 4 \\ 5 \end{matrix} \right\} U_1$

⑦ Augmented loop incidence matrix ( $\hat{C}$ )

	Basic element loop					
		A	B	C	D	E
$\hat{C} =$	1	1	0	0	-1	-1
	2	0	1	0	-1	-1
	3	0	0	1	0	-1
	4	0	0	0	1	0
	5	0	0	0	0	1



Direction of fictitious cutset is same as the direction of link involved in it.


Basic cutset Element	A	B	C	D	E	F
1	1	0	0	0	0	0
2	0	1	0	0	0	0
3	0	0	1	0	0	0
4	0	0	0	1	0	0
5	0	0	1	-1	1	0
6	1	1	1	0	0	1

$$\hat{B} = \begin{bmatrix} U_b & 0 \\ B_d & U_d \end{bmatrix}$$

[This is termed by keep previous same & adding (no. of links) column & it is always +ve to corresp link]
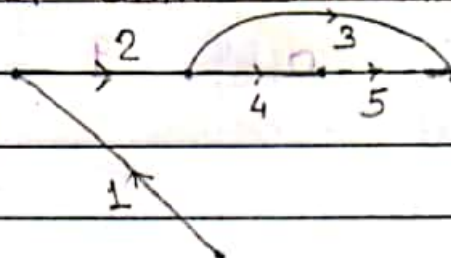
### 5) Basic loop incidence matrix (C)

The basic loop is formed by restoring one link at a time into the tree. Direction of basic loop is decided by the direction of link involved in it.



Bus :-

$$\text{power} = (I_{\text{bus}}^*)^t \cdot E_{\text{bus}}$$

Branch :-

$$\text{power} = (I_{\text{br}}^*)^t \cdot I_{\text{br}}$$

Loop :-

$$\text{power} = (I_{\text{loop}}^*)^t \cdot E_{\text{loop}}$$

\* Property of matrix

If A & B are two matrices

then

$$\textcircled{1} (A \cdot B)^* = A^* \cdot B^*$$



$$\textcircled{2} (A \cdot B)^t = B^t \cdot A^t$$

$$\textcircled{3} (A \cdot B)^{-1} = B^{-1} \cdot A^{-1}$$

Also  $A^* = A$  if it is real matrix

H.W.

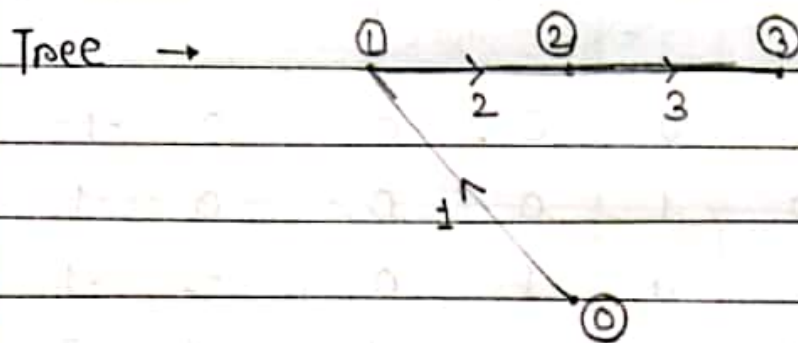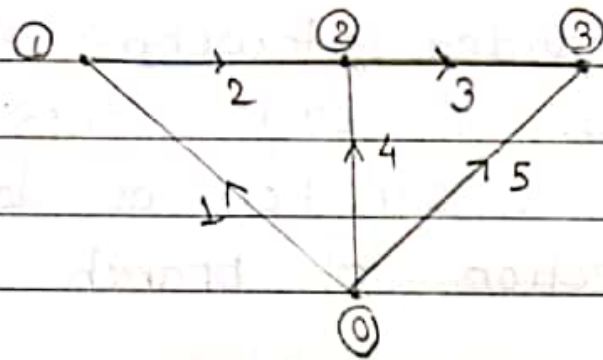Oriented graph of a power system is given below. Select 0 as node reference. 1, 2, 3 is tree form matrices  $A$ ,  $A^1$ ,  $K$ ,  $B$ ,  $B^1$ ,  $C$ ,  $C^1$ . And S.T. (i)  $A_b K t = U$  (ii)  $B_1 \cdot A_b = A_1$



① Element node incidence matrix ( $A^1$ )

nodes elements	①	②	③	
1	1	-1	0	0
2	0	1	-1	0
3	0	0	1	-1
4	1	0	-1	0
5	1	0	0	-1




Basic cutset element	A	B	C	
1	1	0	0	} $B_b$
2	0	1	0	
3	0	0	1	
4	1	1	0	} $B_d$
5	1	1	1	

⑤ Augment cutset incidence matrix ( $B^1$ )

Basic cutset element	A	B	C	D	E
1	1	0	0	0	0
2	0	1	0	0	0
3	0	0	1	0	0
4	1	1	0	1	0
5	1	1	1	0	1

⑥ Basic loop incidence matrix ( $C$ )

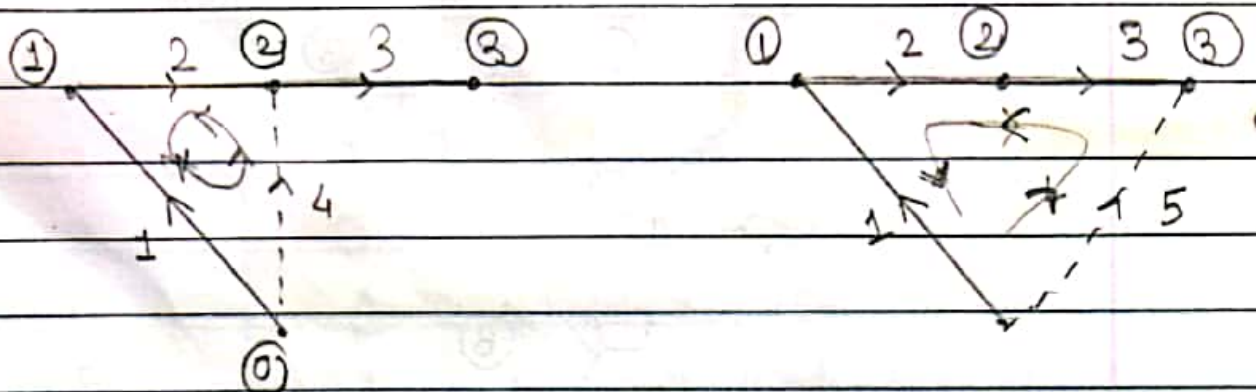

nodes elements	①	②	③	④	⑤
1	1	-1	0	0	0
2	0	1	-1	0	0
3	0	0	1	0	-1
4	0	0	1	-1	0
5	0	0	0	1	-1
6	1	0	0	0	-1

dimension of  $(\hat{A}) = e \times n$

$e$ : no. of element

$n$ : no. of nodes

2) Bus incidence matrix  $[A]$

If we remove any one column of element node incidence matrix then we get 'Bus incidence matrix'.  
Generally prefer ground or zero node

Dimension of  $A = e \times (n-1)$

network of admittance form

$$i + j = [y] v$$

where

$i \rightarrow$  vector of current through element

$v \rightarrow$  —||— voltage across element

$j \rightarrow$  —||— impressed current in ||  
with the elements


$y \rightarrow$  primitive admittance matrix

Diagonal entries of  $y$  represent self admittances of elements & off diagonal entries of  $y$  represent mutual admittances bet<sup>n</sup> the elements

Total power in primitive network is


$$(j^*)^t \cdot v$$



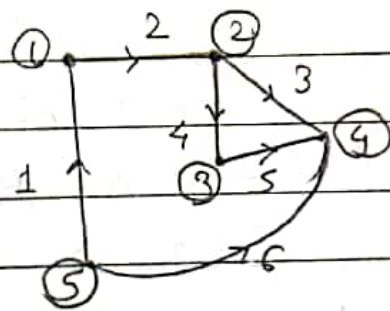

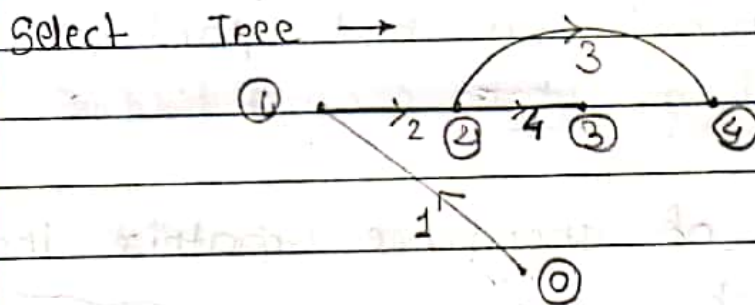3) Branch path incidence matrix (k)

path is formed by moving from a node to reference node in a tree



If  $n$  nodes are present then  $(n-1)$  path will be available

Dimension :  $(n-1) \times (n-1)$

path \ Branch	①	②	③	④
1	-1	-1	-1	-1
2	0	-1	-1	-1
3	0	0	0	-1
4	0	0	-1	0

## \* Network performance eq<sup>n</sup>

### 1) Bus frame of reference

$$E_{bus} = Z_{bus} \cdot I_{bus}$$

↓                      ↳ Impressed bus  
Bus impedance                  current  
matrix

$$I_{bus} = Y_{bus} \cdot E_{bus}$$

↳ Bus admittance matrix

### 2) Branch frame of Reference

$$E_{br} = Z_{br} \cdot I_{br}$$

↳ Impressed branch current

$$I_{br} = Y_{br} \cdot E_{br}$$

↳ Branch admittance matrix

### 3) Loop frame of Reference

$$E_{loop} = Z_{loop} \cdot I_{loop}$$

↓                      ↳ Loop impedance matrix  
Vector of  
Voltage

$$I_{loop} = Y_{loop} \cdot E_{loop}$$

↳ Loop admittance matrix

## ② Bus incidence matrix

nodes elements	①	②	③	
1	-1	0	0	} $A_b$
2	1	-1	0	
3	0	1	-1	
4	0	-1	0	} $A_d$
5	0	0	-1	


$A =$

## ④ Branch path incidence matrix (K)

<del>path</del> Branch	①	②	③
1	-1	-1	-1
2	0	-1	-1
3	0	0	-1

$K =$

## ⑤ Basic cutset incidence matrix (B)

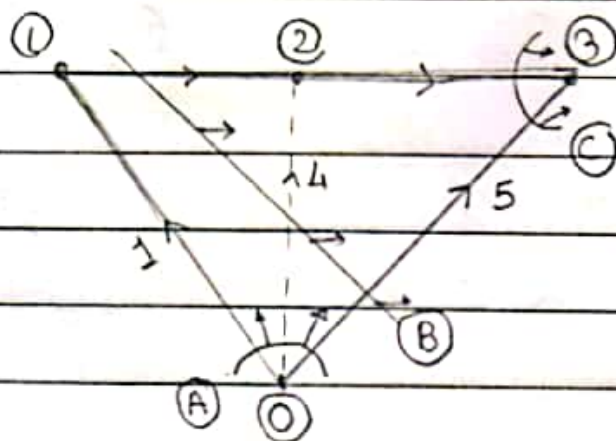



6) Augmented loop incidence matrix ( $\hat{C}$ )

Formation of this matrix  
Fictitious loop (open loop) are taken. An  
open loop involves only one branch & no  
any link. column corresponding to open  
loop are added towards the left of  
the column of basic loops

Direction of loop is decided  
by the direction of branch

Basic loop element	A	B	C	D	E	F
1	1	0	0	0	0	-1
2	0	1	0	0	0	-1
3	0	0	1	0	-1	-1
4	0	0	0	1	1	0
5	0	0	0	0	1	0
6	0	0	0	0	0	1

$$\hat{C} = \begin{bmatrix} U_b & C_b \\ 0 & U_l \end{bmatrix}$$

proof :-

$$\begin{bmatrix} -1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 1 & -1 & 0 \end{bmatrix} = A_b$$

$$K = \begin{bmatrix} -1 & -1 & -1 & -1 \\ 0 & -1 & -1 & -1 \\ 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & 0 \end{bmatrix}$$

$$K^t = \begin{bmatrix} -1 & 0 & 0 & 0 \\ -1 & -1 & 0 & 0 \\ -1 & -1 & 0 & -1 \\ -1 & -1 & -1 & 0 \end{bmatrix}$$

$$A_b \cdot K^t = \begin{bmatrix} -1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 1 & -1 & 0 \end{bmatrix} \cdot \begin{bmatrix} -1 & 0 & 0 & 0 \\ -1 & -1 & 0 & 0 \\ -1 & -1 & 0 & -1 \\ -1 & -1 & -1 & 0 \end{bmatrix}$$

$$A_b \cdot K^t = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

#### 4) Basic cutset incidence matrix (B)


A cutset is group of minimum no. of elements which when removed from the graph divides the graph into two parts, such that restoration of any one element [of cutset] makes the two parts connected.

ex. of cutset (1, 2), (1, 6) & etc

A cutset which involves only one branch is called 'Basic cutset'  $(n-1)$  from which (1, 6) is basic cutset. corresponding to each branch, there will be one basic cutset.

no. of branches = nodes - 1

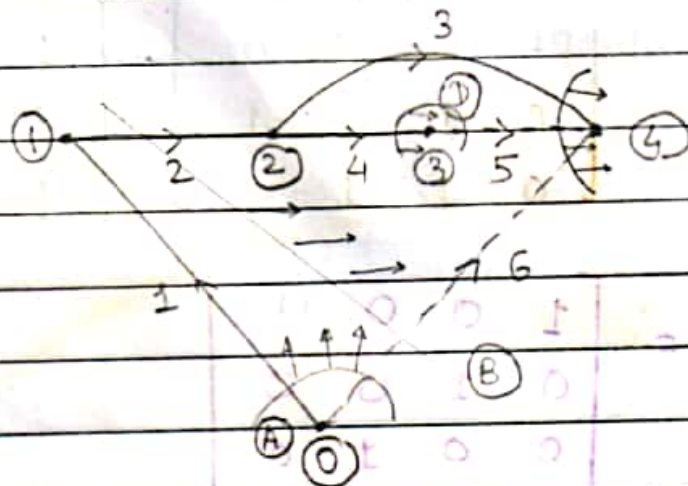The direction of basic cutset is decided by, the direction of branch involved in it.





$Z_{pq} \rightarrow$  impedance of the element

performance equation  $\rightarrow$

Apply KVL to circuit,

$$E_p + E_{pq} - Z_{pq} \cdot i_{pq} = E_q$$

$$E_p - E_q + E_{pq} = Z_{pq} \cdot i_{pq}$$

$$V_{pq} + E_{pq} = Z_{pq} \cdot i_{pq}$$

This is a performance eq<sup>n</sup> in impedance form

performance eq<sup>n</sup> for primitive nlcw in impedance form can be written as,

$$V + e = [Z] i$$

where

$V \rightarrow$  vector of voltage across the elements

$e \rightarrow$  vector of source voltages in series with the elements

$i \rightarrow$  vector of current through elements

$Z \rightarrow$  primitive impedance matrix

[The total power in primitive nlcw is given by  $(i^*)^T \cdot e$ ]

$$C_{ij} = 1$$


If  $i$ th element is a part  $j$ th loop & their direction are same element & loop

$$C_{ij} = -1$$

If  $i$ th element is a part  $j$ th loop & their direction are opposite

$$C_{ij} = 0$$

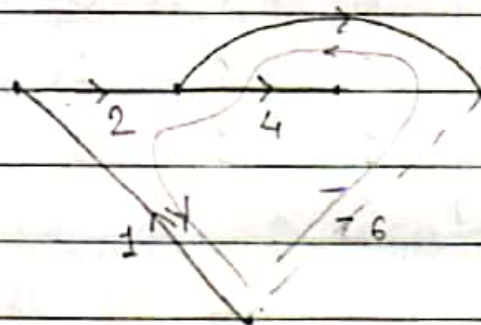If  $i$ th element is not a part of  $j$ th loop



	Basic Loop Element	F	F	
or ex 1	1	0	-1	} $C_b$
	2	0	-1	
	3	-1	-1	
ex (e-n+1)	4	1	0	} $u_a$
ex [(e-n+1)]	5	1	0	
	6	0	1	


## \* Primitive Network

A group of unconnected elements is called primitive network

An element can be represented either in impedance form or in admittance form
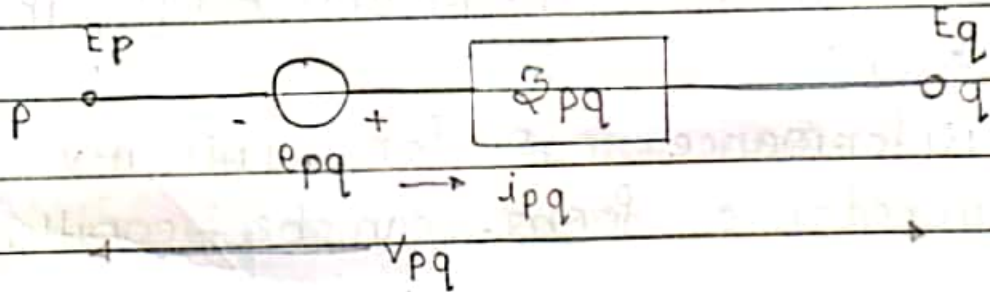
### 1) Impedance form of representing an element

In impedance form an element connected between points  $p$  &  $q$  is represented as,



Here,

$E_p, E_q \rightarrow$  Voltage at point  $p$  &  $q$  resp

$V_{pq} \rightarrow$  Voltage across the element connected bet<sup>n</sup>  $p$  &  $q$

$i_{pq} \rightarrow$  current through the element

$e_{pq} \rightarrow$  source voltage in series with the element